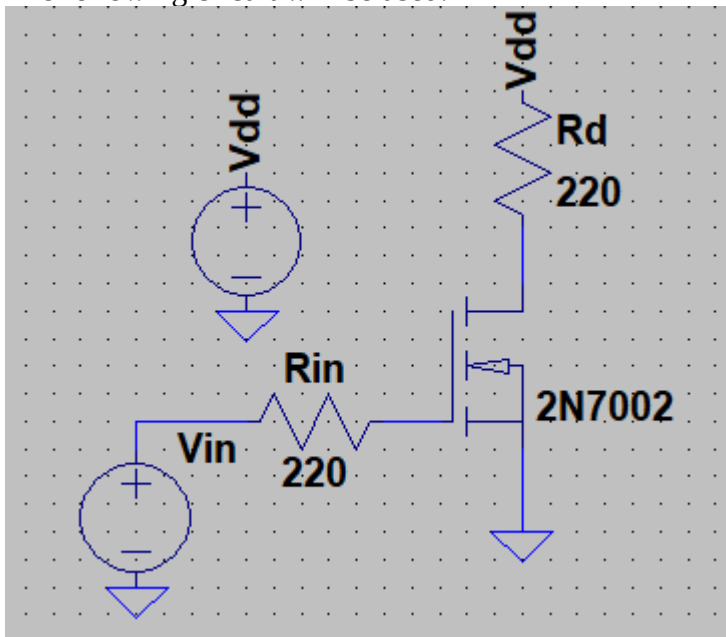


Part 1 I_D vs. V_{DS} plot of a MOSFET


The following circuit will be used:



Real values were used for the resistors so that practical application and testing could be applied.

2N7000 is the MOSFET that will be used. An N-channel with a threshold voltage of .8V minimum and 3V maximum.


Produced the following simulation:

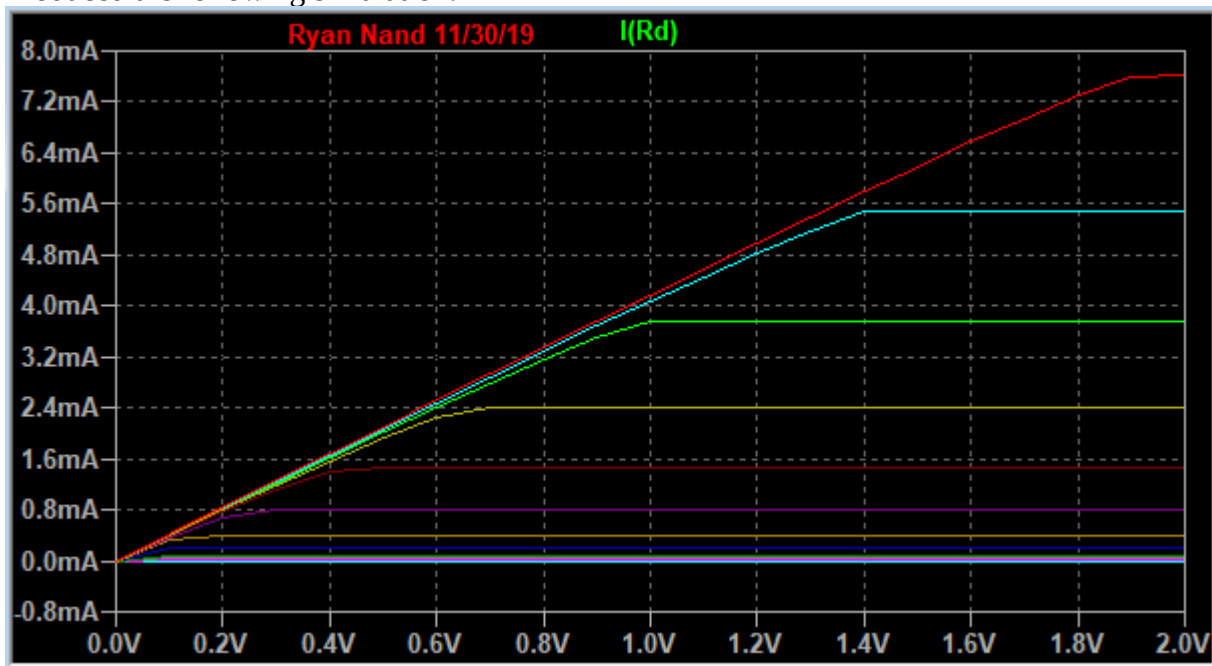

$V_{GS} = 0$ to 1.9

Part 2 Biased MOSFETs

Two resistor bias:

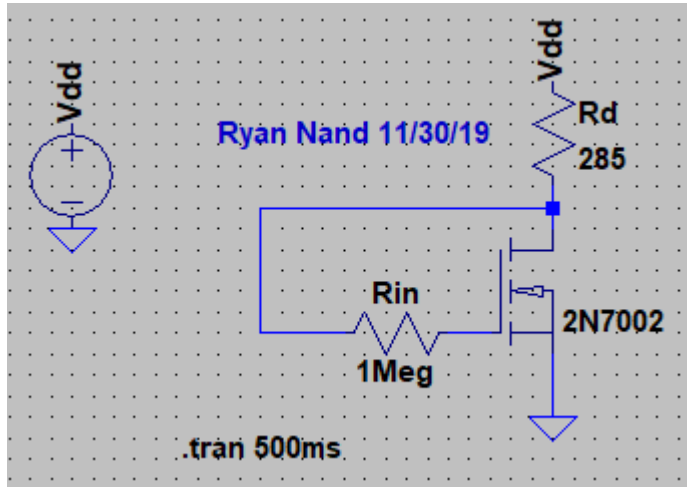



$$V_{DD} = 5V$$

$$I_D = .0657(V_{DS} - V_T)^2$$

$$V_{DS} = V_{GS}$$

$$V_{DS} = V_{DD} - I_D R_D$$

Here the $V_{GS} = 2V$

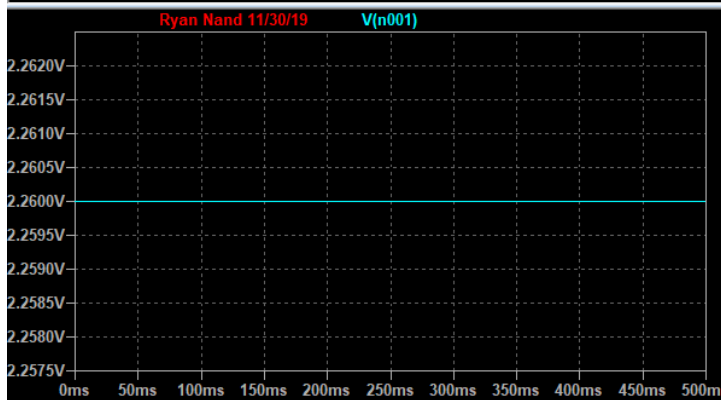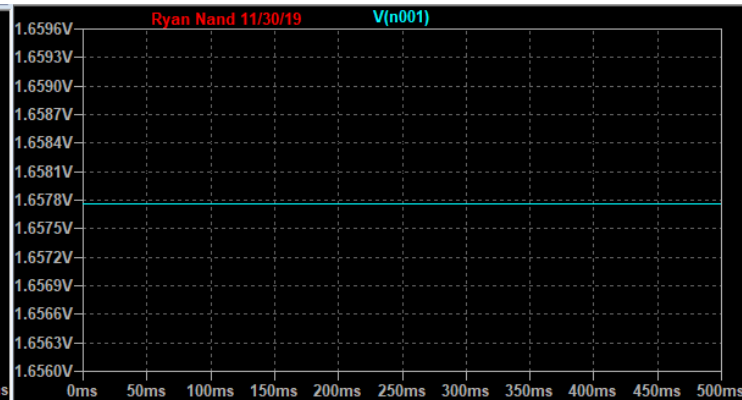

Above from left to right: normal V_T and V_T -20% respectively.
Left is V_T is +20%.
The change in value is as expected.

Four resistor bias:

