

# Laboratory #2: System Identification of a 2nd Order System through Step Response

Report by:

Lee Brady

Ryan Nand

James Ward

Nic Knoblich


Date of Report submission: 04/20/2020

ECE 317 - Signals and Systems III


Department of Electrical and Computer Engineering

Portland State University

Instructor: Professor Richard Tymerski

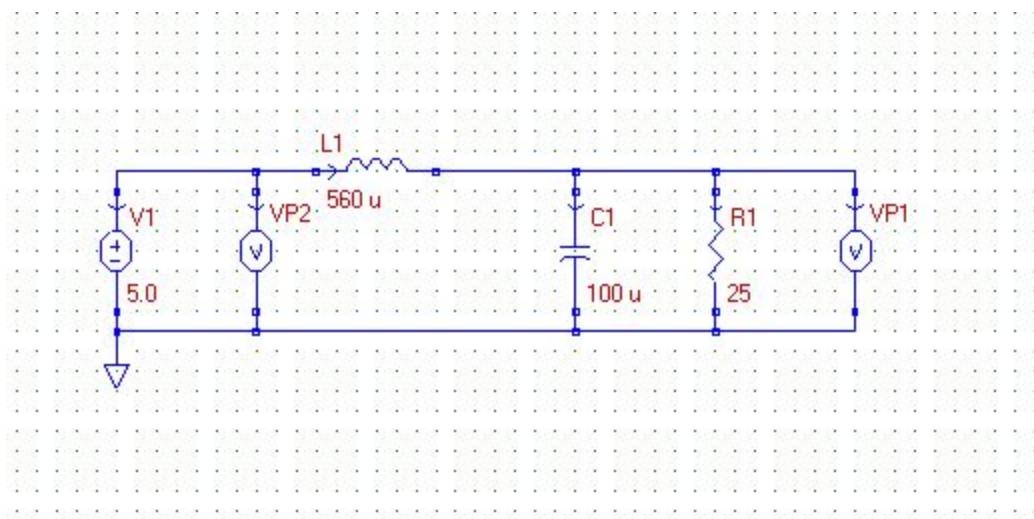

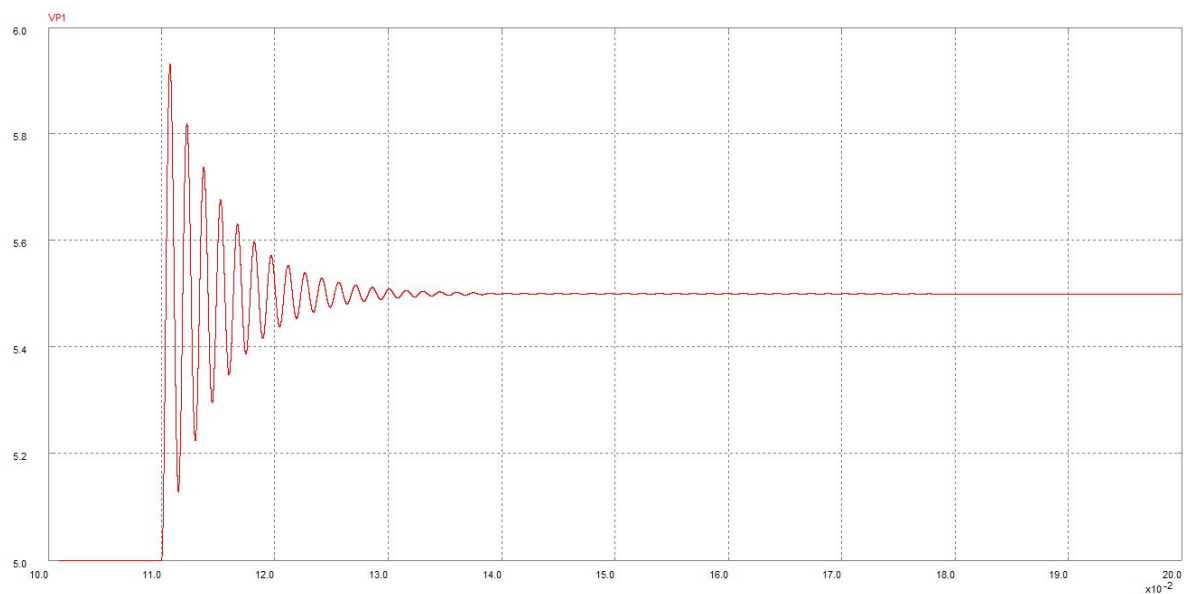The figure above shows our PECS schematic of an LCR network used for this lab.



The figure above shows the voltage (VP1) across the 25  $\Omega$  resistor from our PECS schematic.

Overshoot	$c'_{max}$	5.931 V
Steady State Voltage	$c'_{final}$	5.5 V

As the table above shows, our max overshoot is 5.931 V and the steady state voltage is 5.5 V.

$$c_{max} = c'_{max} - c'_0$$

$$c_{max} = 0.931 \text{ V}$$

$$c_{final} = c'_{final} - c'_0$$

$$c_{final} = 0.5 \text{ V}$$

$$\%OS = \frac{C_{max}-C_{final}}{C_{final}} \times 100 \Rightarrow \frac{0.931-0.5}{0.5} \times 100 = 86.2\%$$

$$\zeta = \frac{-\ln(\%OS/100)}{\sqrt{\pi^2 + \ln^2(\%OS/100)}} \Rightarrow \frac{-\ln(86.2/100)}{\sqrt{\pi^2 + \ln^2(86.2/100)}} = 0.047$$

$$T's = 0.1168s$$

$$0.12942$$

$$19.42$$

$$T_s = T's - \text{step time} \Rightarrow 0.1168 - 0.11 = 6.8ms$$

$$K = \frac{\Delta c}{\Delta v} = \frac{C_{final}-C_o}{V_{final}-V_o} \Rightarrow \frac{5.5-5.0}{5.5-5.0} = 1$$

LCR transfer function derivation:

$$Z_L = sL \text{ and } Z_C = \frac{1}{sC}$$

Using KCL and the relations of the impedances above we get the following:

$$\frac{V_o-0}{R} + \frac{V_o-0}{Z_C} + \frac{V_o-V_i}{Z_L} = 0$$

Isolate input and output.

$$V_o \left( \frac{1}{R} + \frac{1}{Z_C} + \frac{1}{Z_L} \right) = \frac{V_i}{Z_L}$$

Combine impedances.

$$V_o \left( \frac{Z_L Z_C + R Z_L + R Z_C}{R Z_C Z_L} \right) = \frac{V_i}{Z_L}$$

Divide for transfer function.

$$\frac{V_o}{V_i} = \frac{R Z_C}{Z_L Z_C + R Z_L + R Z_C}$$

Now looking only at the right hand side of the transfer function, plug in the impedance values.

$$\frac{R \frac{1}{sC}}{sL \frac{1}{sC} + R sL + R \frac{1}{sC}}$$

Multiply by sC.

$$\frac{R}{sL + RsLsC + R}$$

Simplify.

$$\frac{R}{s^2RLC + sL + R}$$

Divide by R.

$$\frac{1}{s^2LC + s\frac{L}{R} + 1}$$

Now we have the desired transfer function.

$$\frac{1}{s^2LC + s\frac{L}{R} + 1} = \frac{K}{a_1s^2 + a_2s + 1} = \frac{K}{(\frac{s}{\omega_n})^2 + 2\xi\frac{s}{\omega_n} + 1}$$

From the relationships of the transfer functions above  $K = 1$ .

$$a_1 = \frac{1}{\omega_n^2} = LC$$

Therefore,  $\omega_n = \frac{1}{\sqrt{LC}}$ .

$$a_2 = 2\xi\frac{1}{\omega_n} = \frac{L}{R}$$

Plug in  $\omega_n$ .

$$2\xi(\sqrt{LC}) = \frac{L}{R}$$

Therefore,  $\xi = \frac{L}{2R\sqrt{LC}}$ .

Transfer Function Parameters	PECS Simulation Derived Values	Symbolic Transfer Function	Evaluated Transfer Function
$\xi$	.047	$\frac{L}{2R\sqrt{LC}}$	.047
$\omega_n$	<del>12515.6</del> 4380	$\frac{1}{\sqrt{LC}}$	4225.77
K	1	1	1

```

% Component values
L = 560e-06;
C = 100e-06;
R = 25;

% Transfer function parameters
K = 1;      % DC gain
a1 = L*C;   % Coefficient of s^2 of denominator
a2 = L/R;   % Coefficient of s^1 of denominator

% Transfer function
tf_LCR = tf(K, [a1, a2, 1]);

% t is a vector of 1000 time values linearly spaced between 0 and .2
t = linspace(0, .2, 1000);
% Create step function
u = 5*ones(length(t), 1);
% Create the time for step excitation
step_time = .11;
% n accounts for all time after excitation
n = find(t >= step_time);
% The input after the excitation time initiates
u(n) = u(n) + .5; % A 10% step

% Simulation of the LCR network
y = lsim(tf_LCR,u,t);

% The output response
figure(1)
plot(t,y)
title('Output response including the large-signal start-up transient')

% Isolate the small-signal step response
c_prime_0 = y(n(1)-1); % Initial output before the step
ys = y(n) - c_prime_0; % Small signal output response
ts = t(n) - step_time; % Small signal response times

% Small signal step response
figure(2)
plot(ts, ys)
title('Step response')

% Small signal step response metrics
stepinfo(ys,ts)

```

### LCR Low-Pass Filter Matlab Code

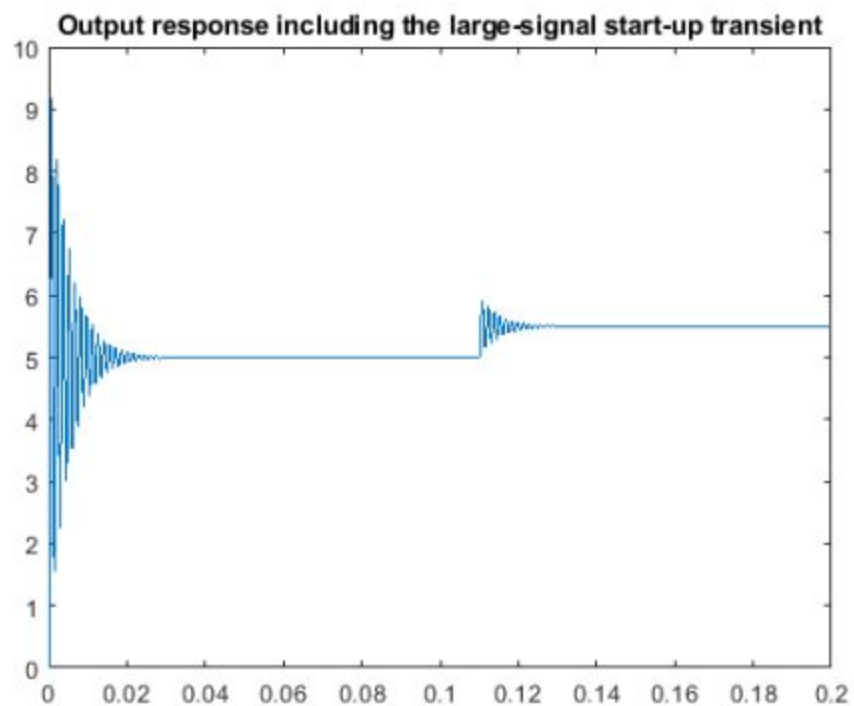


Fig. 1 Output Response LCR Filter

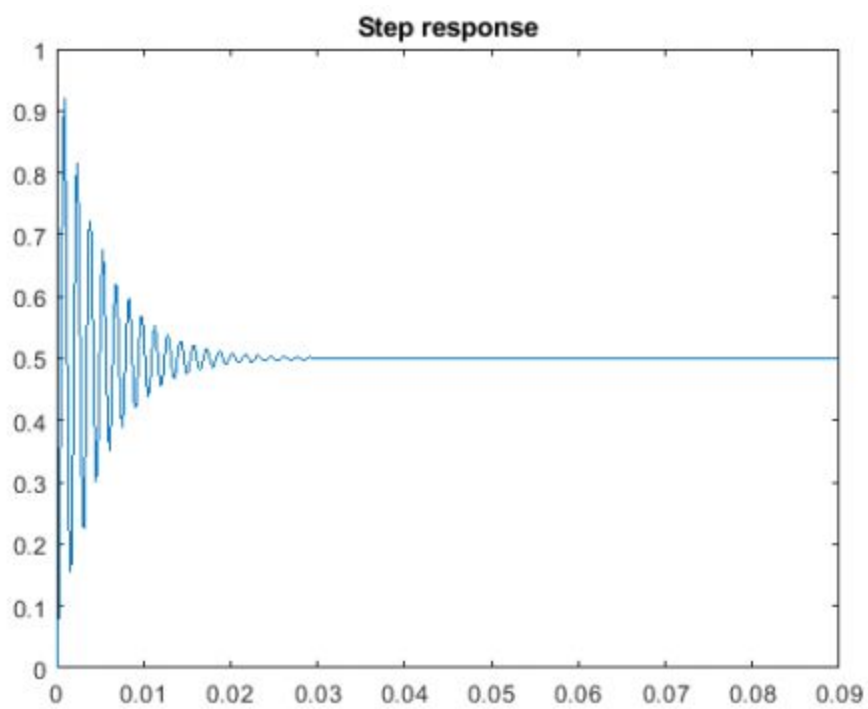


Fig. 2 Step Response of LCR Filter

```

RiseTime: 2.9428e-04
SettlingTime: 0.0188
SettlingMin: 0.1539
SettlingMax: 0.9187
Overshoot: 83.7408
Undershoot: 1.2966e-07
Peak: 0.9187
PeakTime: 9.1091e-04

```

Output of Matlab stepinfo function

Response Feature	From PECS	From Matlab
%OS	86.2	83.74
T <sub>s</sub> (taken from plots when V<0.39)	<del>8ms</del> 19.42	<del>7.5ms</del> 19.5

Derivation of transfer function with r<sub>L</sub> included:

Adding in Series Resistor with inductor called r<sub>L</sub> Leads to voltage divider equation

$$\frac{V_o}{V_{IN}} = \frac{R}{CLRs^2 + (Cr_L R + L)s + r_L + R}$$

Transfer function with simplification applied:

$$\frac{V_o}{V_{IN}} = \frac{R}{CLRs^2 + (Cr_L + L)s + R} = \frac{1}{CLs^2 + (Cr_L + \frac{L}{R})s + 1}$$

*Appreciable change in DC gain?*

No change in DC gain after approximation r<sub>L</sub> + R = R.

*Appreciable change in undamped natural frequency?*

No change in undamped natural frequency.

*Appreciable change in damping factor?*

This factor is what gets changed the most from transfer function above

$$2\xi\frac{1}{\omega_n}=Cr_L+\frac{L}{R}$$

$$\xi=\frac{C R r_L+L}{2 R \sqrt{L C}}$$



## Lab 2 Grading Sheet

1. Task 1: Your PECS schematic_____	/1
2. Task 4:	
(i) Plot_____	/1
(ii) $c'_{max}$ _____	/1
(iii) $c'_{final}$ _____	/1
3. Task 5:	
(i) $c_{max}$ _____	/1
(ii) $c_{final}$ _____	/1
4. Task 6:	
(i) %OS_____	/2
(ii) $\zeta$ _____	/2
5. Task 7:	
(i) $T'_s$ _____	0 /1
(ii) $T_s$ _____	0 /1
6. Task 8: $K$ _____	/2
7. Task 9:	
(i) LCR transfer function derivation_____	/2
(ii) $K$ as a function of elements_____	/1
(iii) $a1$ as a function of elements_____	/1
(iv) $a2$ as a function of elements_____	/1
(v) completed table_____	5.5 /6
8. Task 10: Your complete Matlab code_____	/2
9. Task 11:	
(i) Matlab plot 1_____	/1
(ii) Matlab plot 2_____	/1
10. Task 12:	
(i) Output of Matlab <i>stepinfo</i> function_____	/1
(ii) Completed table_____	1 /2
11. Task 13:	
(i) Derivation of transfer function with $rL$ included_____	/2
(ii) Transfer function with simplification applied_____	/1
(iii) Appreciable change in DC gain?_____	/1
(iv) Appreciable change in undamped natural frequency?_____	/1
(v) Appreciable change in damping factor?_____	/1
Report:_____	/7
<b>Total:</b> _____	41.5 /45